

Connect the Transformer Using the Following Information:

Circuit Voltage: 4,800

Transformer 1

HV – 4,800 / 8,300v


KVA - 75 KVA

LV – 120 / 240v


POL -

Using industry standards fill in the correct polarity

A _____
B _____
C _____
N _____

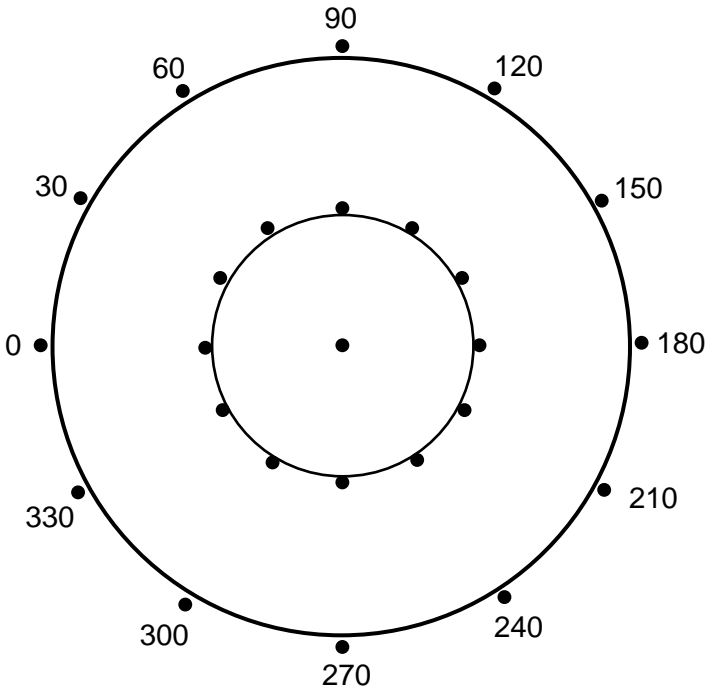

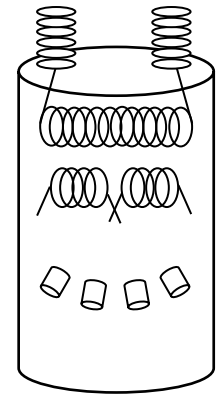Use Outer Circle for Primary Vector - Label A, B, & C
Use Inner Circle for Secondary Vector - Label a, b, & c



Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Customer Needs: 120/240

Connect the Transformer Using the Following Information:


Transformer 1

HV – 19,900 / 34,500v **KVA** - 50 KVA
LV – 120 / 240v **POL** -


Using industry standards fill in the correct polarity

Circuit Voltage: 34,500

A _____
B _____
C _____
N _____

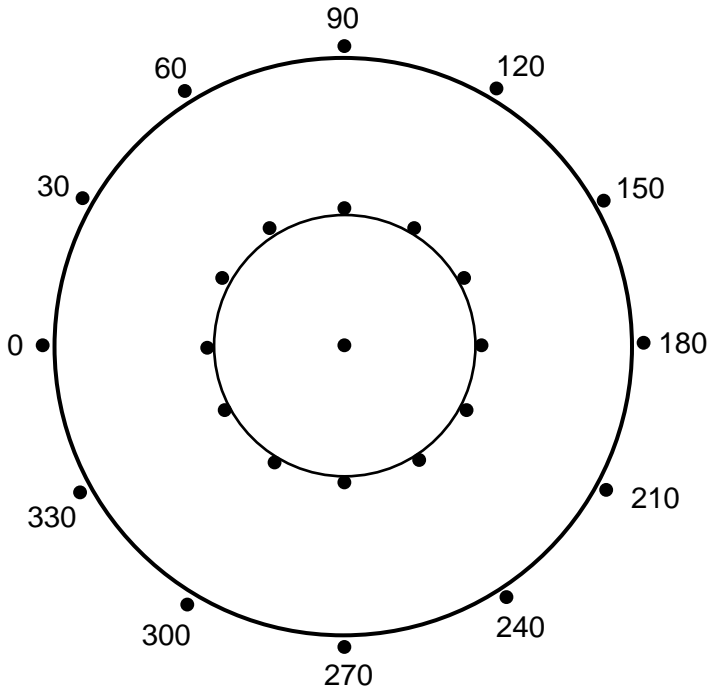

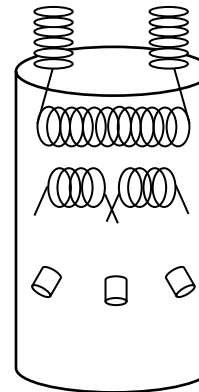Use Outer Circle for Primary Vector - Label A, B, & C
Use Inner Circle for Secondary Vector - Label a, b, & c



Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Customer Needs: 120/240

Connect the Transformer Using the Following Information:

Transformer 1

HV – 4,160 / 7,200v **KVA** - 50 KVA
LV – 120 / 240v **POL** -


Using industry standards fill in the correct polarity

Transformer 2

HV – 4,160 / 7,200v **KVA** - 50 KVA
LV – 120 / 240v **POL** -

Transformer 3

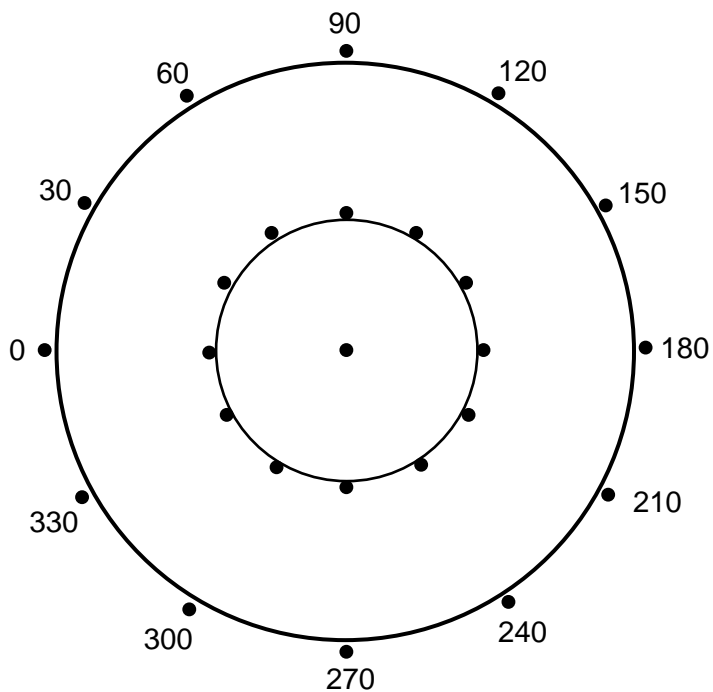
HV – 4,160 / 7,200v **KVA** - 50 KVA
LV – 120 / 240v **POL** -



Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Circuit Voltage: 7,200

A _____
B _____
C _____
N _____

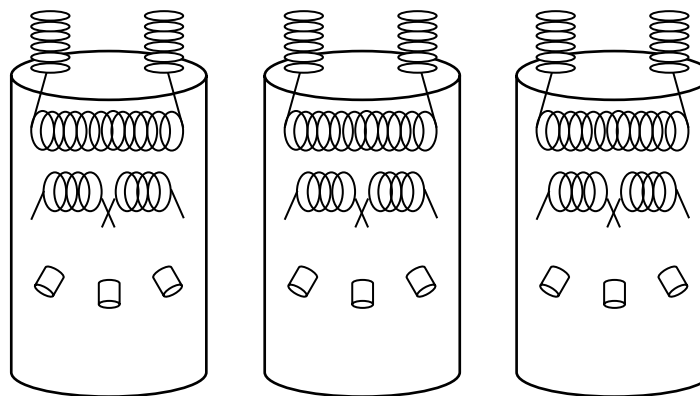

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 12,000v **KVA** - 25 KVA
LV – 120 / 240v **POL** –


Using industry standards fill in the correct polarity

Transformer 2

HV – 12,000v **KVA** - 25 KVA
LV – 120 / 240v **POL** –


Transformer 3

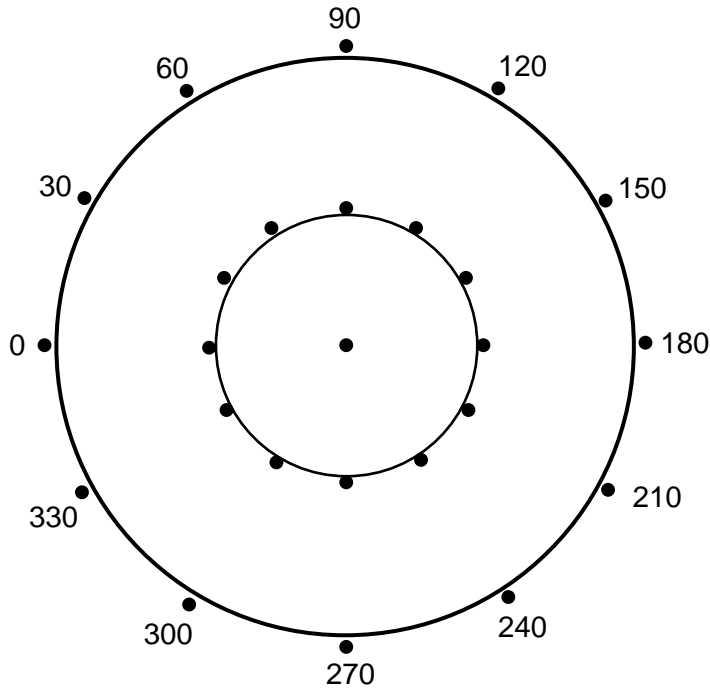HV – 12,000v **KVA** - 25 KVA
LV – 120 / 240v **POL** –



Circuit Voltage: 12,000

A _____
B _____
C _____
N _____

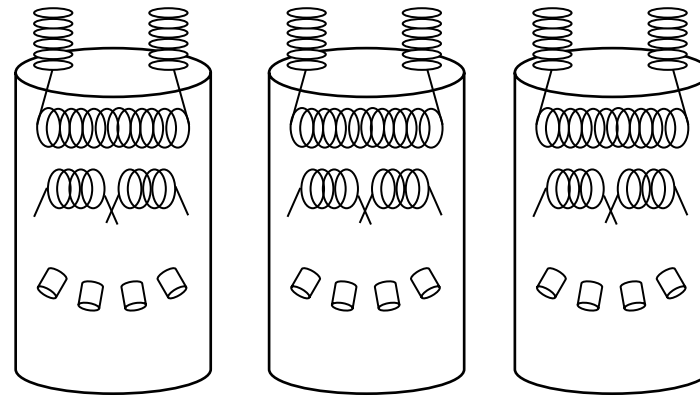

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/208 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 11,500 / 19,900v **KVA** - 15 KVA
LV – 120 / 240v **POL** –

Using industry standards fill in the correct polarity

Transformer 2


HV – 11,500 / 19,900v **KVA** - 15 KVA
LV – 120 / 240v **POL** –

Transformer 3


HV – 11,500 / 19,900v **KVA** - 15 KVA
LV – 120 / 240v **POL** –

Circuit Voltage: 19,900

A _____
B _____
C _____
N _____

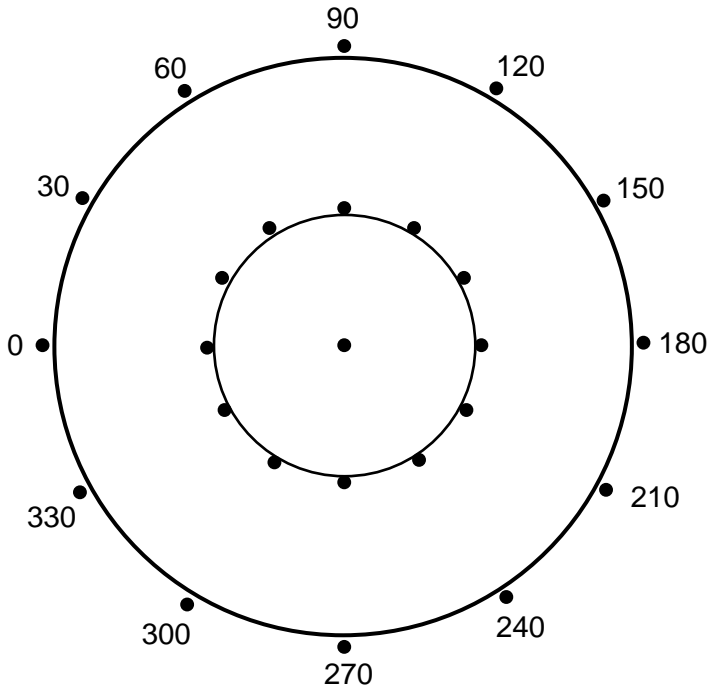

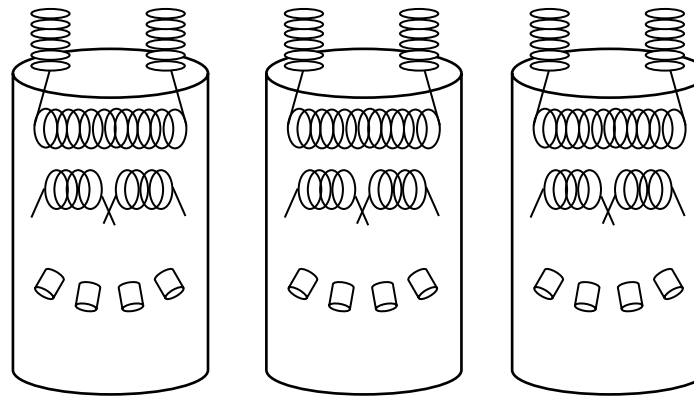Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 120/208 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 14,400 / 24,900v **KVA** - 50 KVA
LV – 120 / 240v **POL** –


Using industry standards fill in the correct polarity

Transformer 2

HV – 14,400 / 24,900v **KVA** - 50 KVA
LV – 120 / 240v **POL** –


Transformer 3

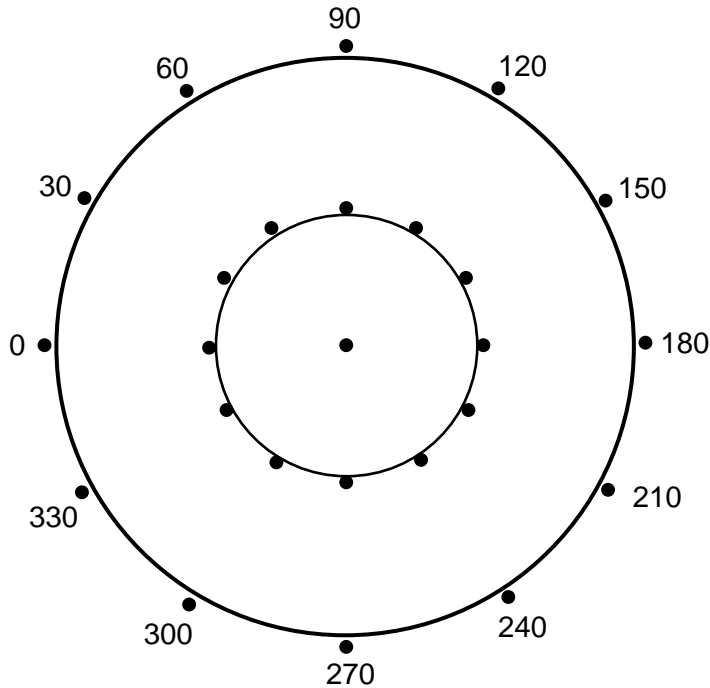HV – 14,400 / 24,900v **KVA** - 50 KVA
LV – 120 / 240v **POL** –



Circuit Voltage: 24,900

A _____
B _____
C _____
N _____

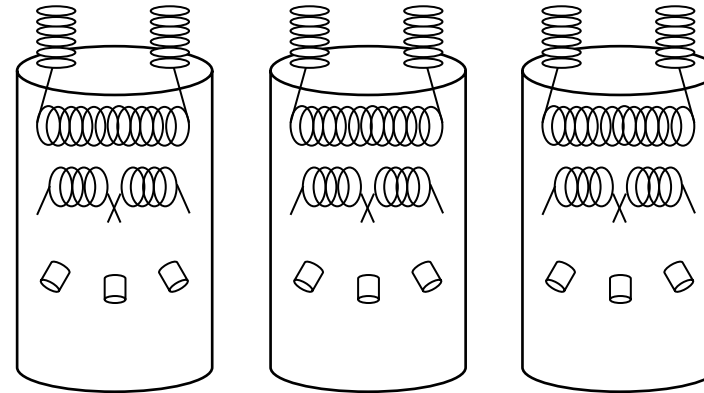

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 240 3Ø Grounded leg

Connect the Transformer Using the Following Information:

Transformer 1

HV – 2,400 / 4,160v **KVA** - 25 KVA
LV – 120 / 240v **POL** –

Using industry standards fill in the correct polarity

Transformer 2



HV – 2,400 / 4,160v **KVA** - 75 KVA
LV – 120 / 240v **POL** –

Transformer 3

HV – 2,400 / 4,160v **KVA** - 25 KVA
LV – 120 / 240v **POL** –

Circuit Voltage: 2,400

A _____
B _____
C _____
N _____

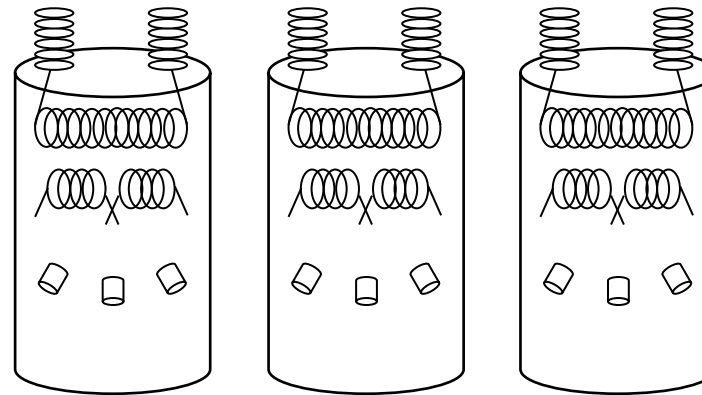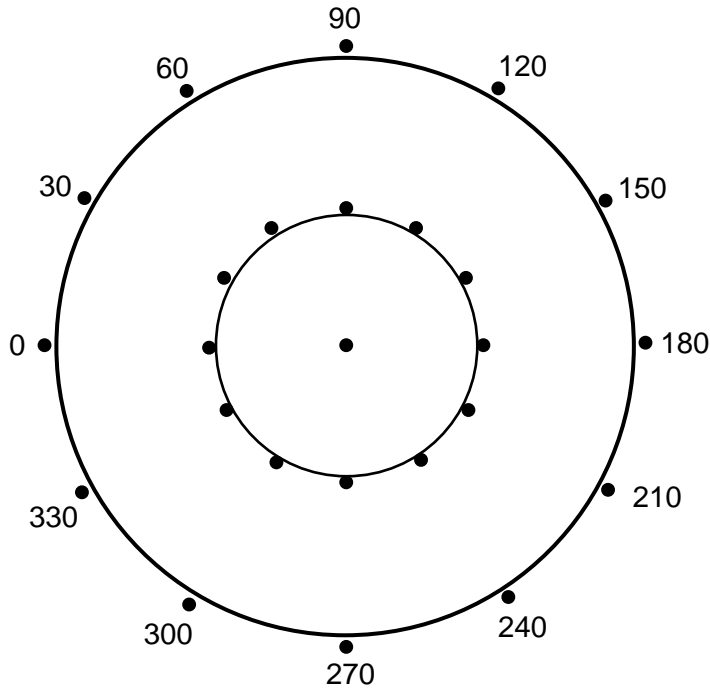

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 2,400 / 4,160v **KVA** - 37.5 KVA
LV – 240 / 480v **POL** –


Using industry standards fill in the correct polarity

Transformer 2


HV – 2,400 / 4,160v **KVA** - 37.5 KVA
LV – 240 / 480v **POL** –

Circuit Voltage: 4,160

A _____
B _____
C _____
N _____

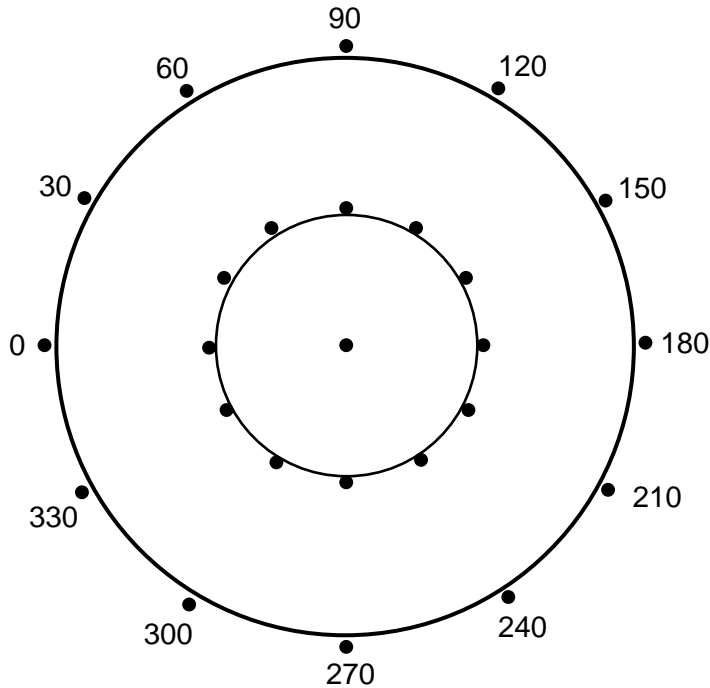

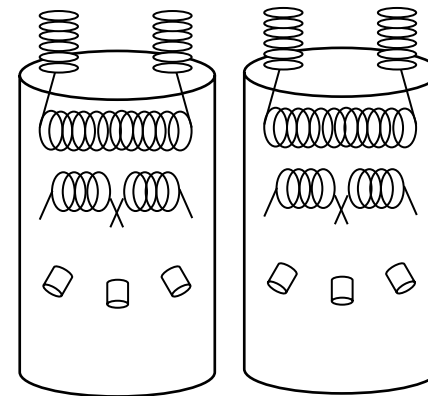Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 480 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 7,600v KVA - 50 KVA
 LV – 120 / 240v POL –


Using industry standards fill in the correct polarity

Transformer 2

HV – 7,600v KVA - 50 KVA
 LV – 120 / 240v POL –


Transformer 3

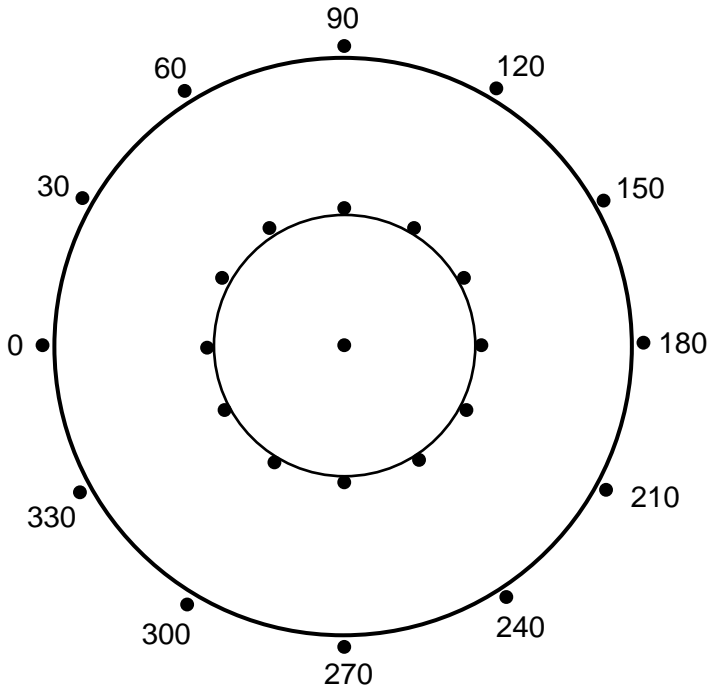HV – 7,600v KVA - 50 KVA
 LV – 120 / 240v POL –



Circuit Voltage: 7,600

A _____
 B _____
 C _____
 N _____

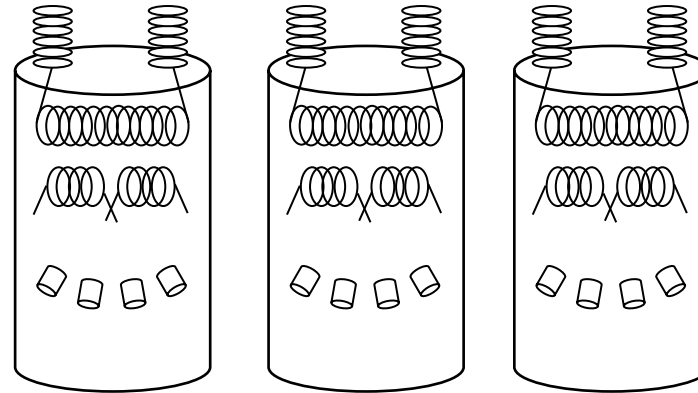

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
 b _____
 c _____
 n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 14,400 / 24,900v **KVA** – 37.5 KVA
LV – 120 / 240v **POL** –


Using industry standards fill in the correct polarity

Transformer 2

HV – 14,400 / 24,900v **KVA** – 75 KVA
LV – 120 / 240v **POL** –


Transformer 3

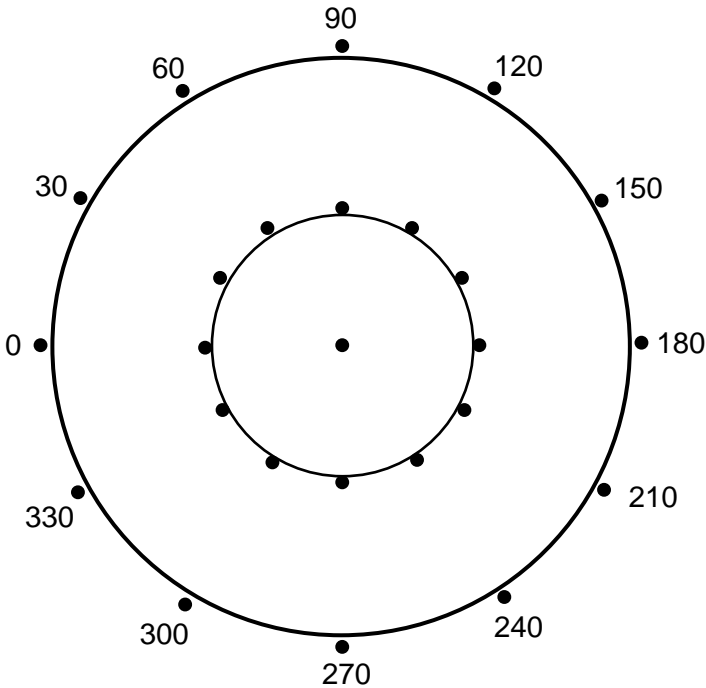HV – 14,400 / 24,900v **KVA** – 37.5 KVA
LV – 120 / 240v **POL** –



Circuit Voltage: 24,900

A _____
B _____
C _____
N _____

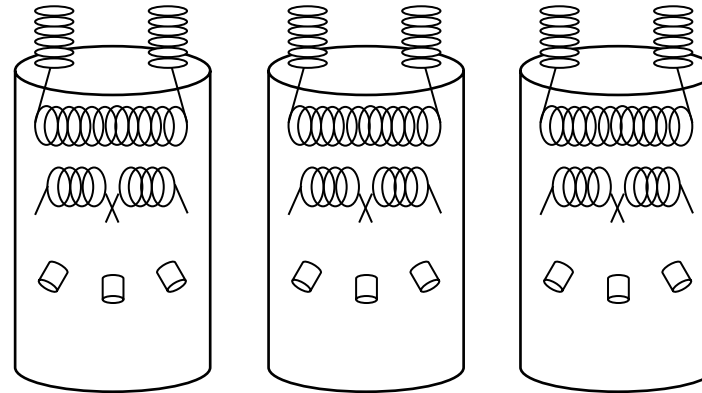

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 13,200 / 22,800v **KVA** - 25 KVA
LV – 120 / 240v **POL** –



Using industry standards fill in the correct polarity

Transformer 2

HV – 13,200 / 22,800v **KVA** - 75 KVA
LV – 120 / 240v **POL** –

Circuit Voltage: 13,200

A _____
B _____
C _____
N _____

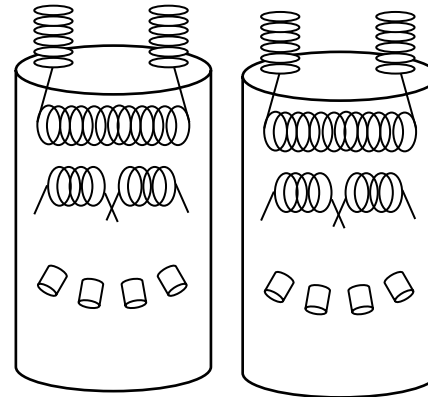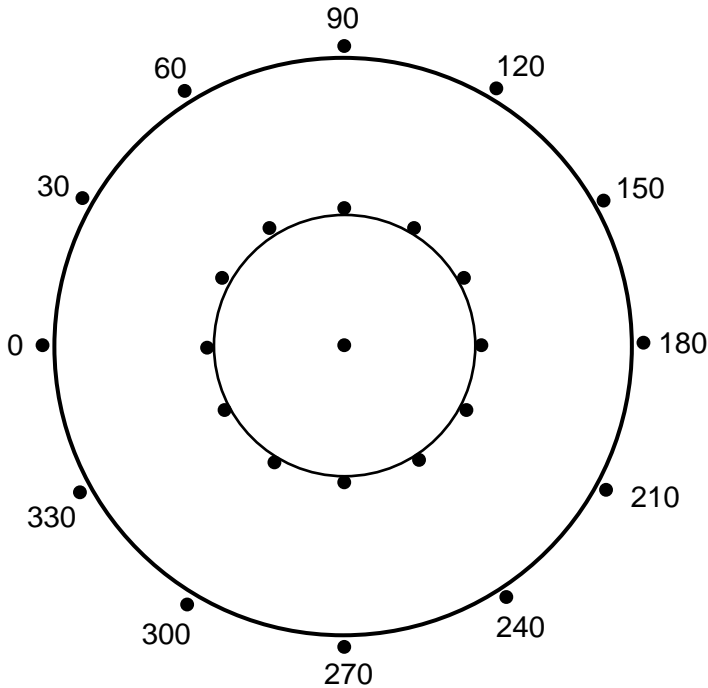

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 2,400 / 4,160v **KVA** – 37.5 KVA
LV – 120 / 240v **POL** –


Using industry standards fill in the correct polarity

Transformer 2

HV – 2,400 / 4,160v **KVA** – 37.5 KVA
LV – 120 / 240v **POL** –


Transformer 3

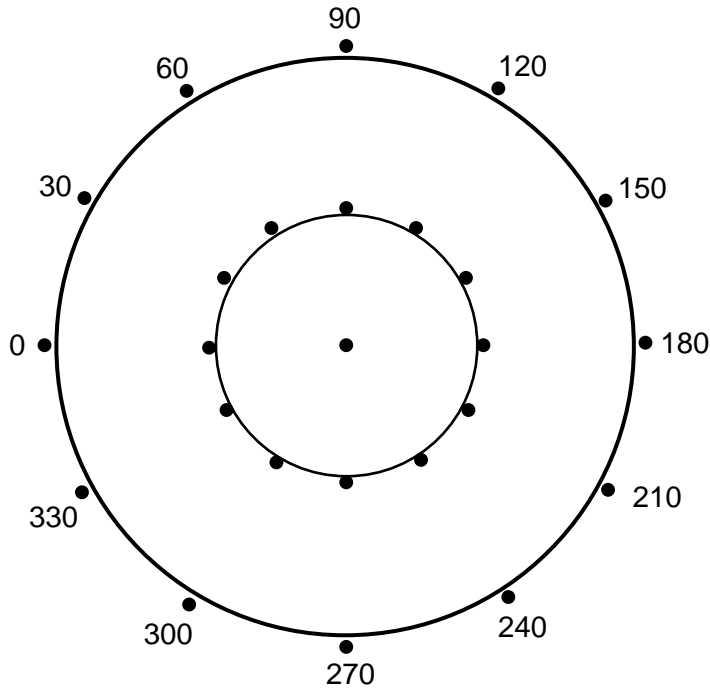HV – 2,400 / 4,160v **KVA** – 37.5 KVA
LV – 120 / 240v **POL** –



Circuit Voltage: 4,160

A _____
B _____
C _____
N _____

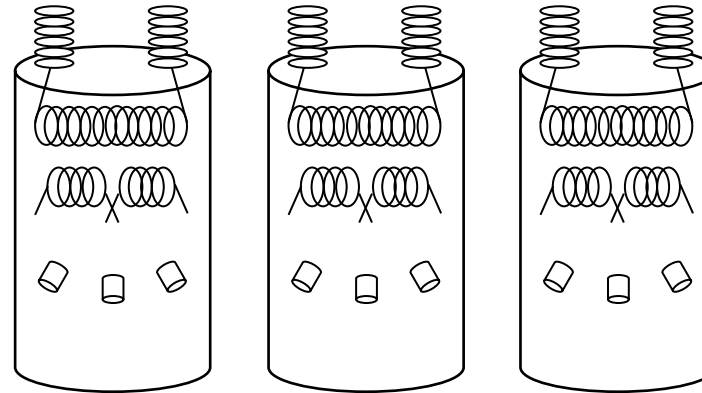

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/208 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 2,400 / 4,160v **KVA** - 250 KVA
LV – 120 / 240v **POL** –


Using industry standards fill in the correct polarity

Transformer 2

HV – 2,400 / 4,160v **KVA** - 250 KVA
LV – 120 / 240v **POL** –


Transformer 3

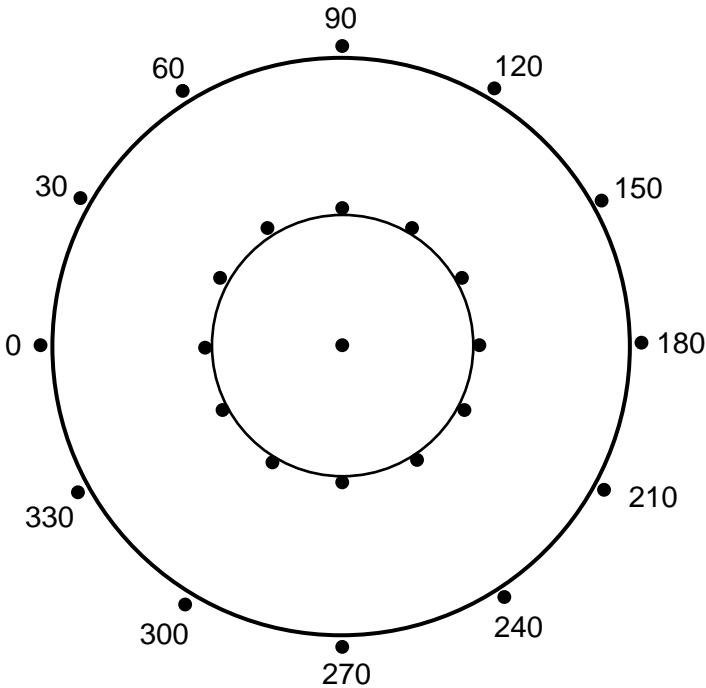HV – 2,400 / 4,160v **KVA** - 250 KVA
LV – 120 / 240v **POL** –



Circuit Voltage: 2,400

A _____
B _____
C _____
N _____

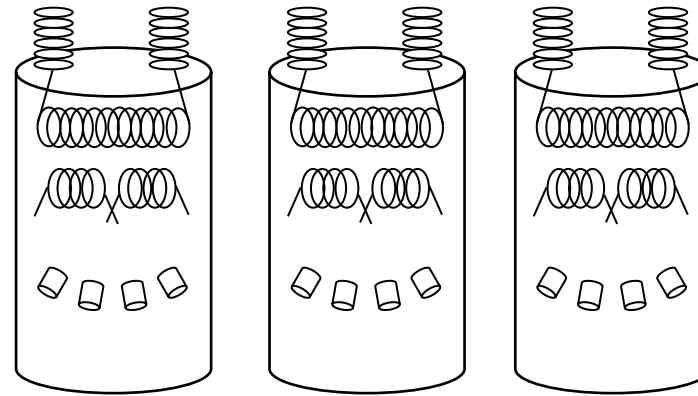

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/208 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 4,160 / 7,200 v **KVA** - 250 KVA

LV – 120 / 240v **POL** –

Using industry standards fill in the correct polarity

Transformer 2


HV – 4,160 / 7,200 v **KVA** - 250 KVA

LV – 120 / 240v **POL** -

Transformer 3


HV – 4,160 / 7,200 v **KVA** - 325 KVA

LV – 120 / 240v **POL** -

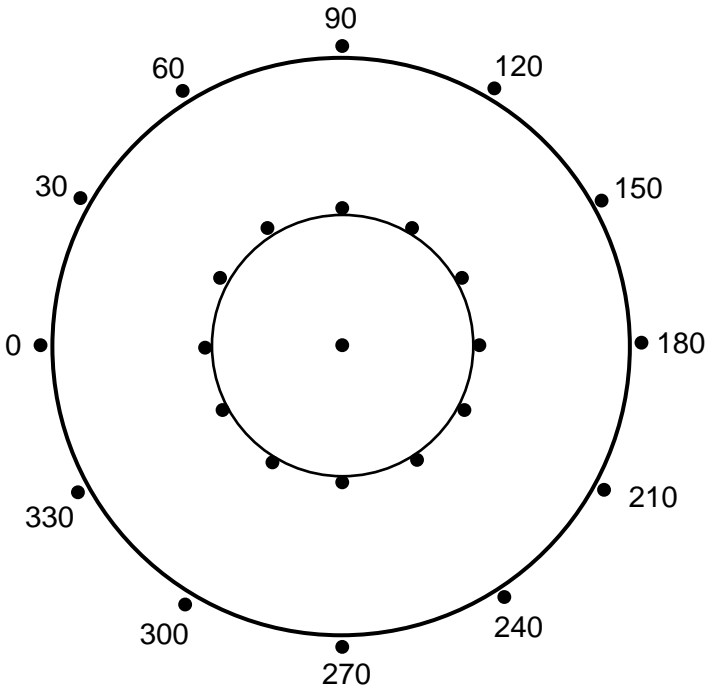

Circuit Voltage: 7,200

A _____
B _____
C _____
N _____

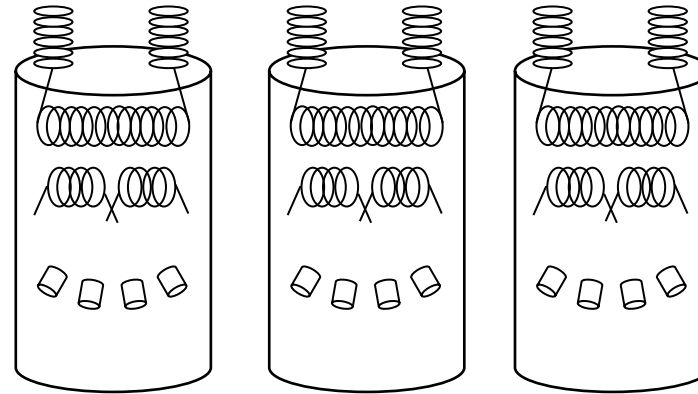

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C

Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 4,800v **KVA** – 15 KVA
LV – 240 / 480v **POL** –

Transformer 2

HV – 4,800v **KVA** – 15 KVA
LV – 240 / 480v **POL** –



Transformer 3

HV – 4,800v **KVA** – 15 KVA
LV – 240 / 480v **POL** –

Using industry standards fill in the correct polarity

Circuit Voltage: 4800

A _____
B _____
C _____
N _____

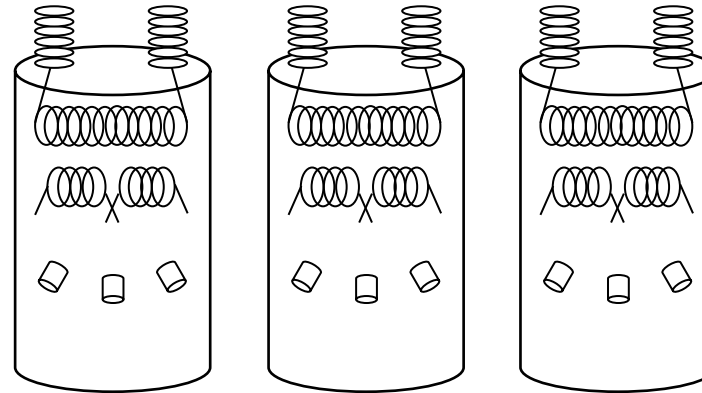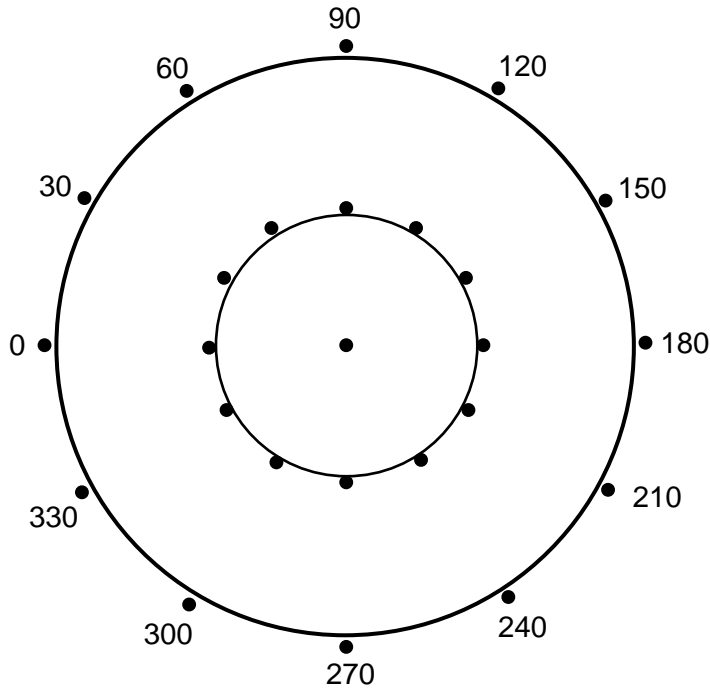

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 480 3Ø


Connect the Transformer Using the Following Information:

Transformer 1
HV – 7,200 / 12,470v **KVA** - 205 KVA
LV – 277v **POL** –

Using industry standards fill in the correct polarity

Transformer 2
HV – 7,200 / 12,470v **KVA** - 205 KVA
LV – 277v **POL** –

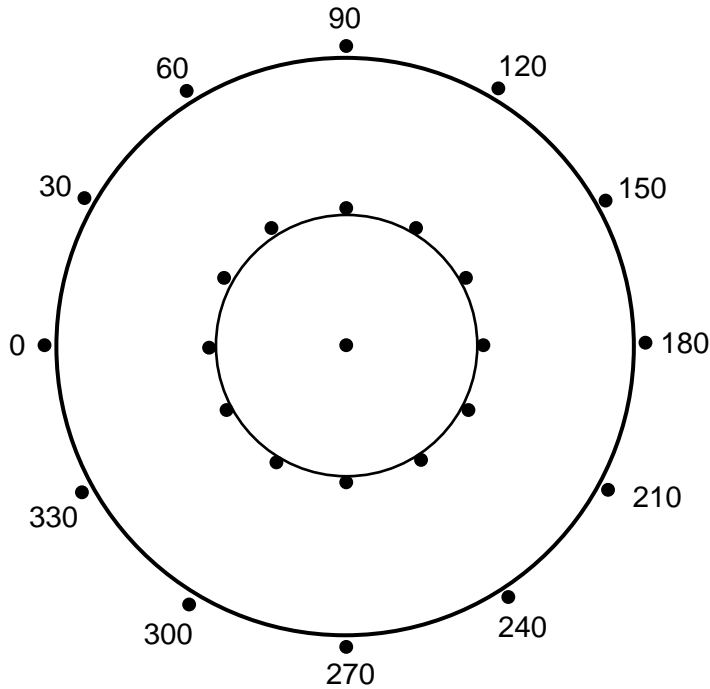
Transformer 3
HV – 7,200 / 12,470v **KVA** - 205 KVA
LV – 277v **POL** –



Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Circuit Voltage: 12,470

A _____
B _____
C _____
N _____

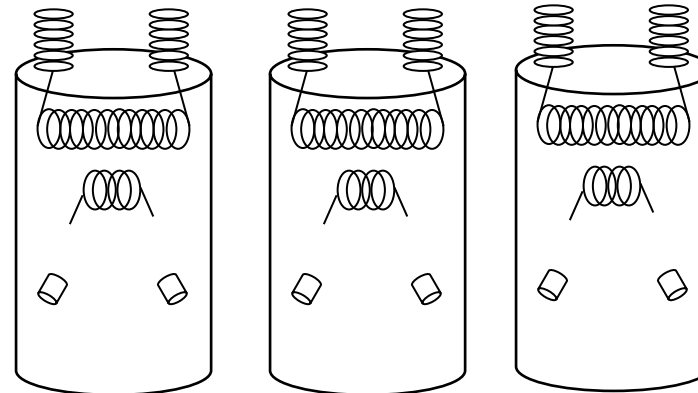

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 277/480 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 120,000v **KVA** - 750 KVA
LV – 7,200v **POL** –

Using industry standards fill in the correct polarity

Transformer 2


HV – 120,000v **KVA** - 750 KVA
LV – 7,200v **POL** –

Transformer 3


HV – 120,000v **KVA** - 750 KVA
LV – 7,200v **POL** –

Circuit Voltage: 120,000

A _____
B _____
C _____
N _____

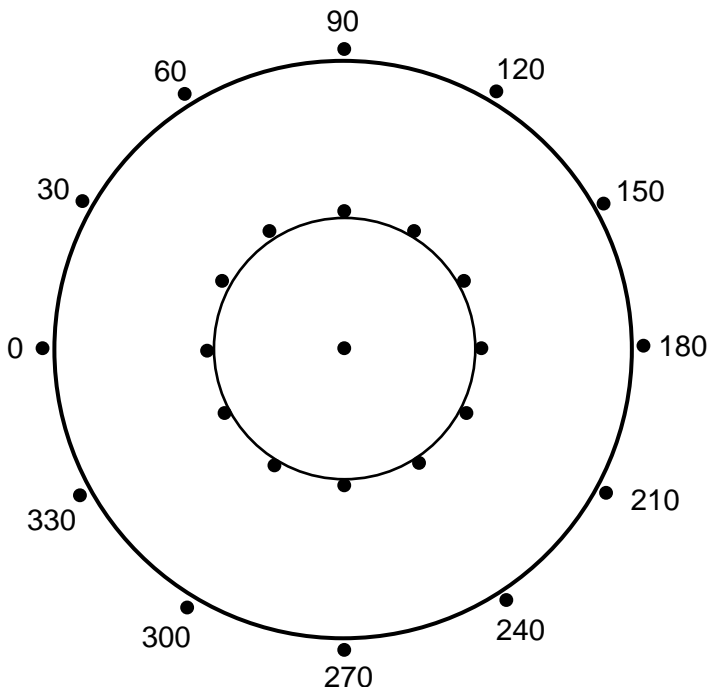

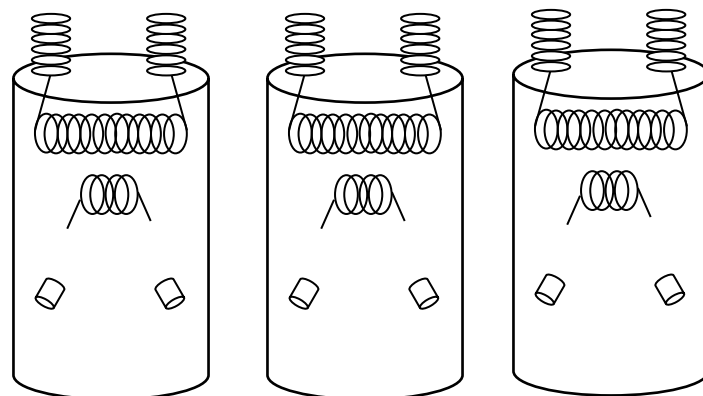Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 7,200/12,470 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 4,160 / 7,200v **KVA** - 50 KVA
LV – 277v **POL** –

Using industry standards fill in the correct polarity

Transformer 2



HV – 4,160 / 7,200v **KVA** - 50 KVA
LV – 277v **POL** –

Transformer 3

HV – 4,160 / 7,200v **KVA** - 50 KVA
LV – 277v **POL** –

Circuit Voltage: 7,200 v

A _____
B _____
C _____
N _____

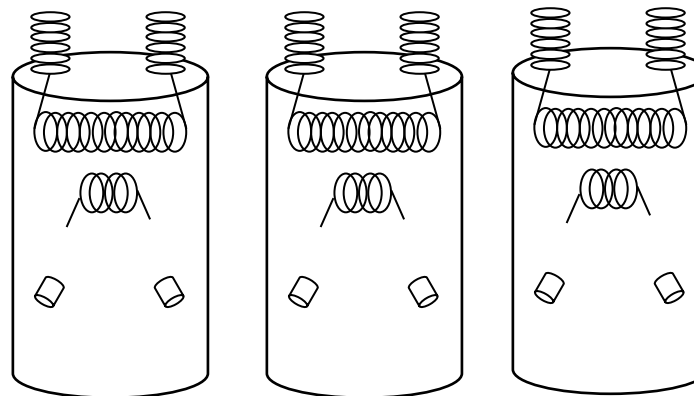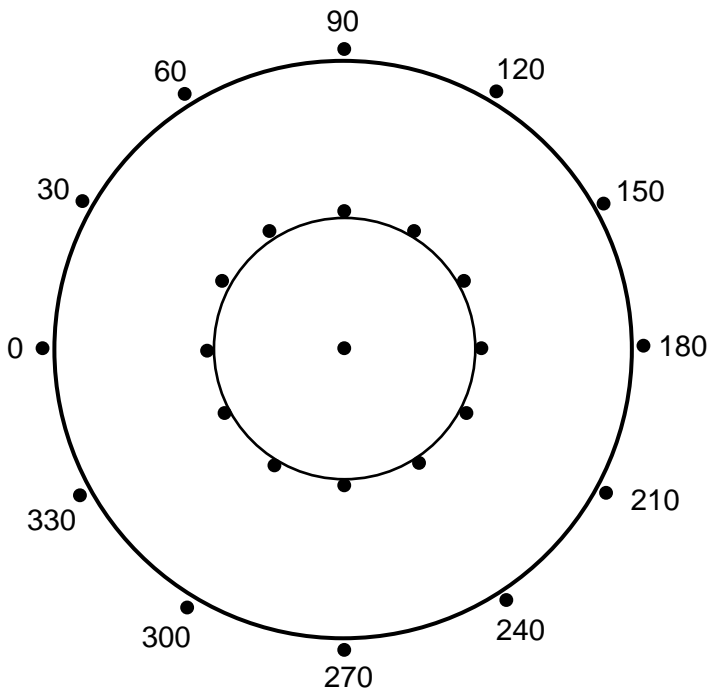

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Customer Needs: 480 3Ø

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Connect the Transformer Using the Following Information:

Transformer 1

HV – 4,000 / 6,900v **KVA** - 150 KVA
LV – 120v **POL** –

Transformer 2

HV – 4,000 / 6,900v **KVA** - 150 KVA
LV – 120v **POL** –



Transformer 3

HV – 4,000 / 6,900v **KVA** - 150 KVA
LV – 120v **POL** –

Using industry standards fill in the correct polarity

Circuit Voltage: 4,000 v

A _____
B _____
C _____
N _____

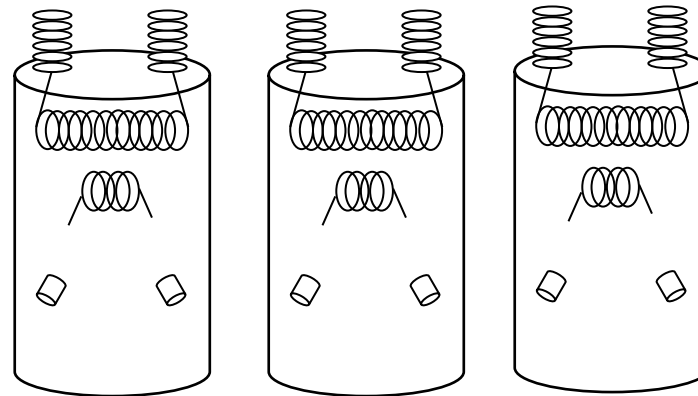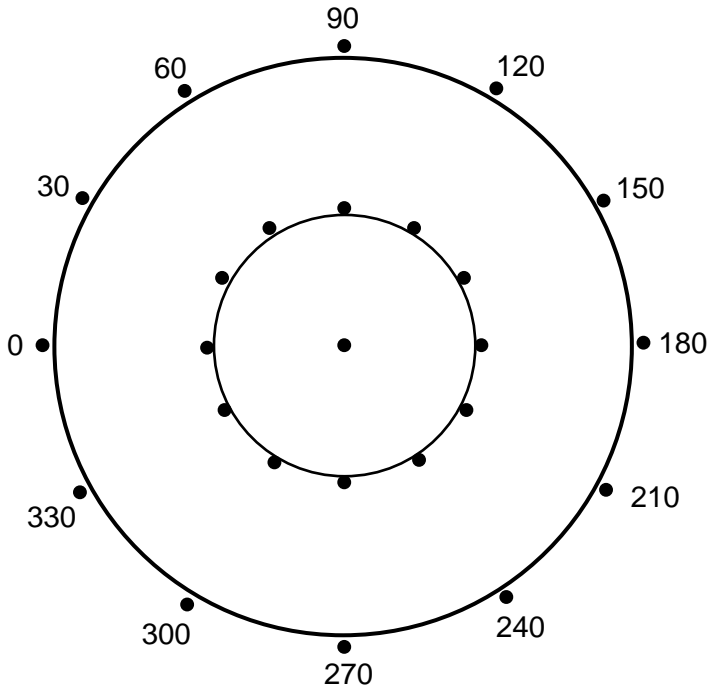

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/208 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 4,160 / 7,200v **KVA** - 75 KVA
LV – 120 / 240v **POL** –


Using industry standards fill in the correct polarity

Transformer 2


HV – 4,160 / 7,200v **KVA** - 25 KVA
LV – 120 / 240v **POL** -

Circuit Voltage: 4,160

A _____
B _____
C _____
N _____

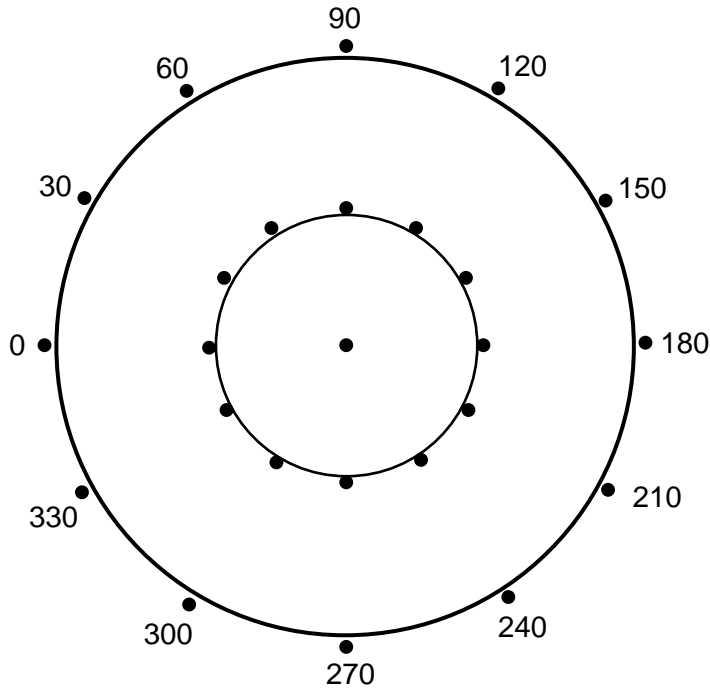

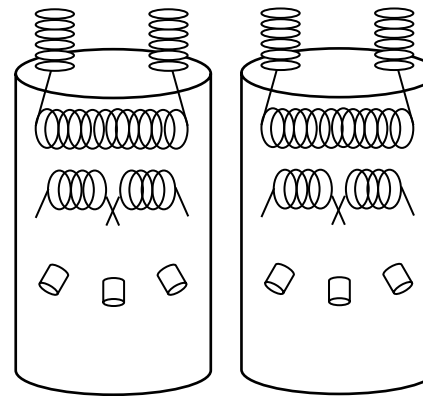Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 120/240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 7,200 / 4,160v **KVA** - 225 KVA
LV – 120 / 240v **POL** –



Using industry standards fill in the correct polarity

Transformer 2

HV – 7,200 / 4,160v **KVA** - 275 KVA
LV – 120 / 240v **POL** –

Circuit Voltage: 7,200 v

A _____
B _____
C _____
N _____

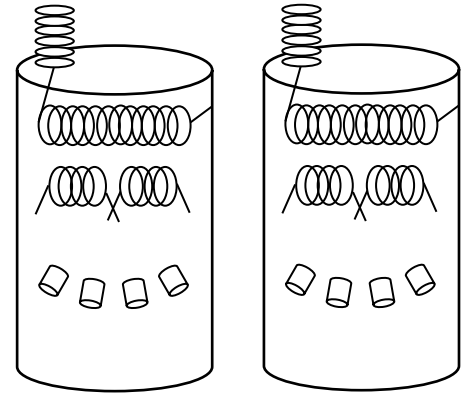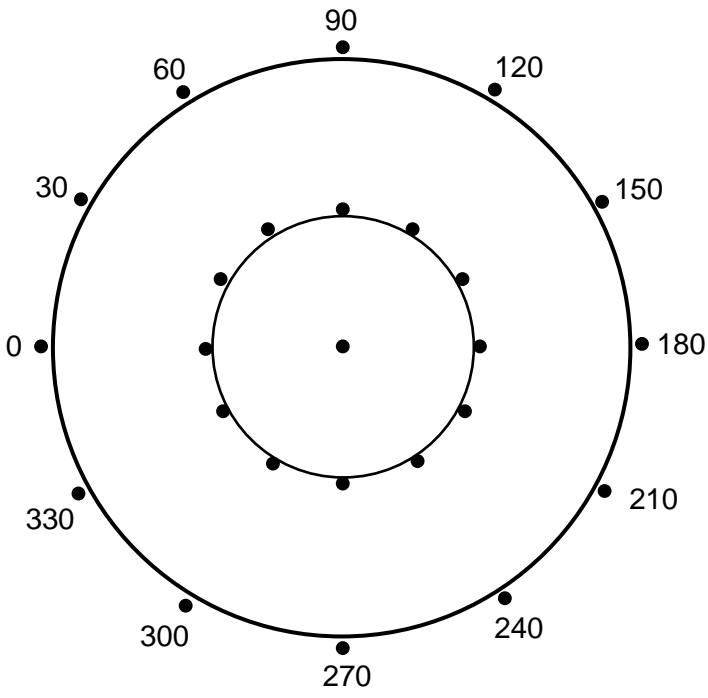

Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/240 3Ø

Connect the Transformer Using the Following Information:

Transformer 1

HV – 7,200 / 4,160v **KVA** - 250 KVA
LV – 240 / 120v **POL** –



Using industry standards fill in the correct polarity

Transformer 2

HV – 7,200 / 4,160v **KVA** - 275 KVA
LV – 240 / 120v **POL** –

Circuit Voltage: 7,200 v

A _____
B _____
C _____
N _____

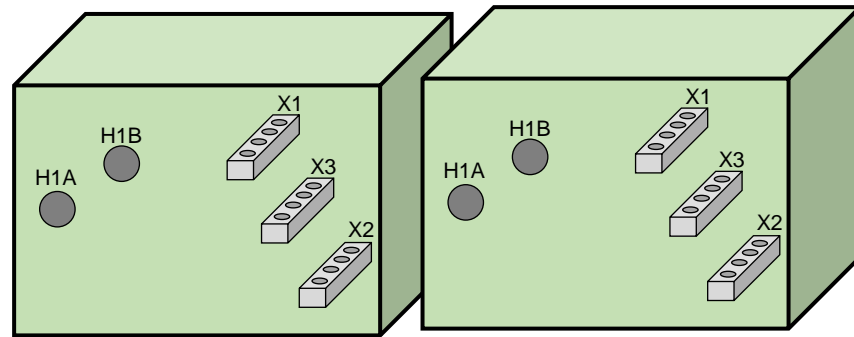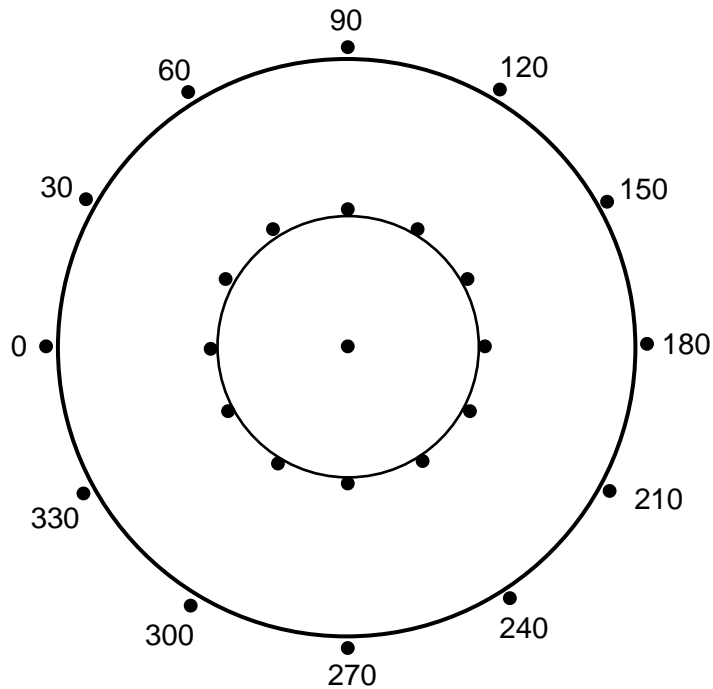

a _____
b _____
c _____
n _____

Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Use Outer Circle for Primary Vector - Label A, B, & C
Use Inner Circle for Secondary Vector - Label a, b, & c

Customer Needs: 120/240 3Ø

Circuit Voltage: 7,200

Connect the Transformer Using the Following Information:

Transformer 1

HV – 7,200v KVA - 25 KVA
 LV – 120 / 240v POL -

Transformer 2


HV – 7,200v KVA - 25 KVA
 LV – 120 / 240v POL -

Transformer 3


HV – 7,200v KVA - 25 KVA
 LV – 120 / 240v POL -

Using industry standards fill in the correct polarity

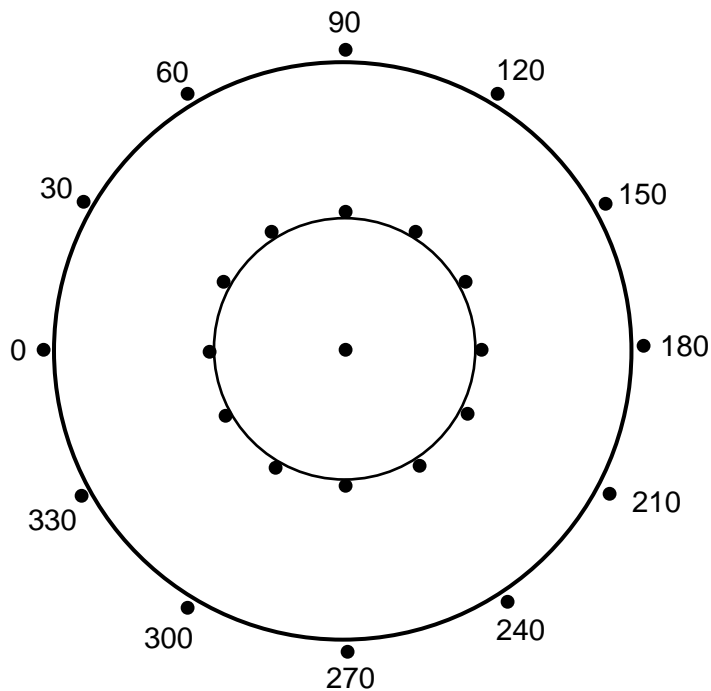Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings



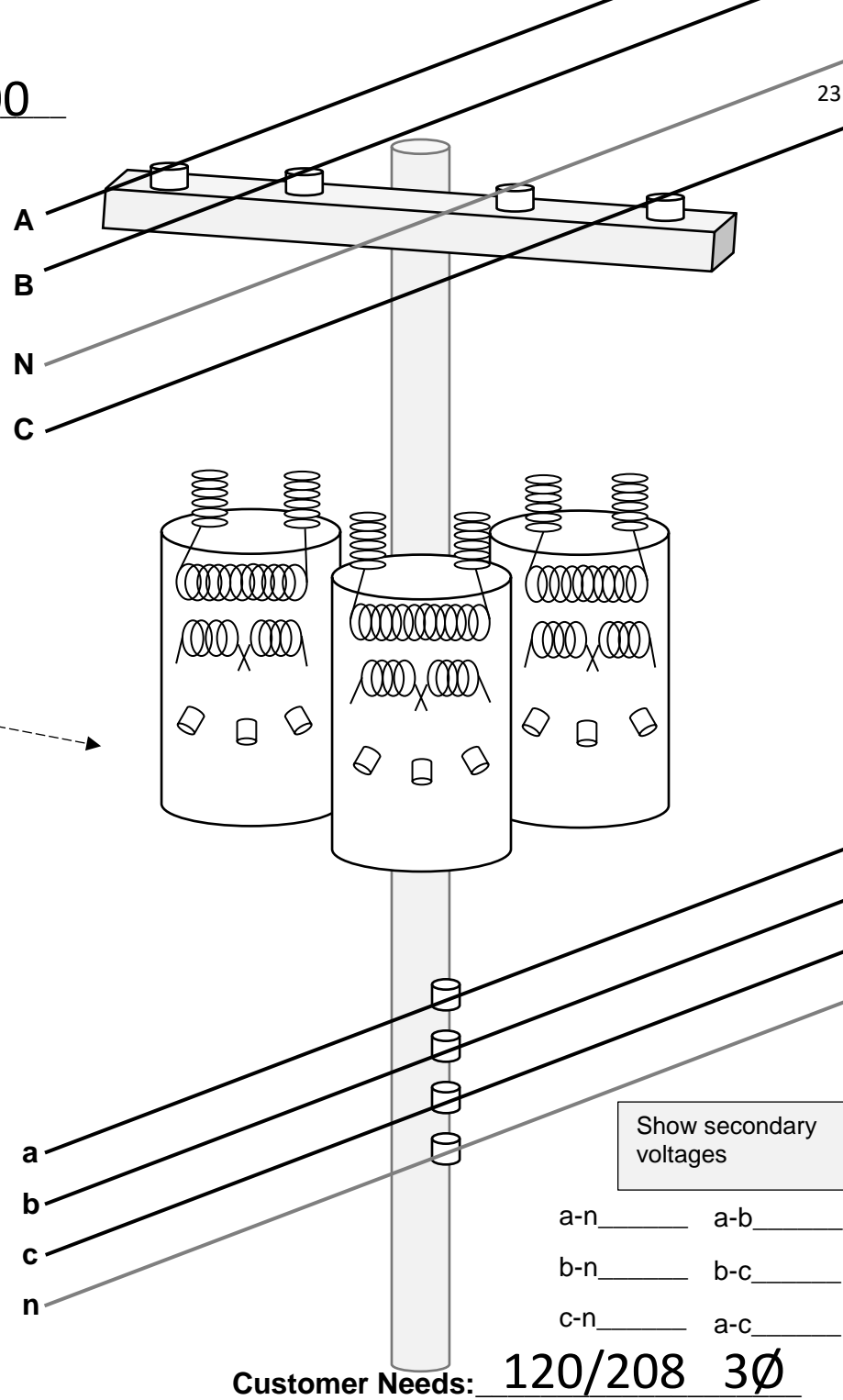Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Customer Needs: 120/208 3Ø

Circuit Voltage: 24,900

Connect the Transformer Using the Following Information:

Transformer 1

HV – 14,400 / 24,900v **KVA** - 225 KVA
LV – 120 / 240v **POL** -

Transformer 2


HV – 14,400 / 24,900v **KVA** - 275 KVA
LV – 120 / 240v **POL** -

Transformer 3


HV – 14,400 / 24,900v **KVA** - 225 KVA
LV – 120 / 240v **POL** -

Using industry standards fill in the correct polarity

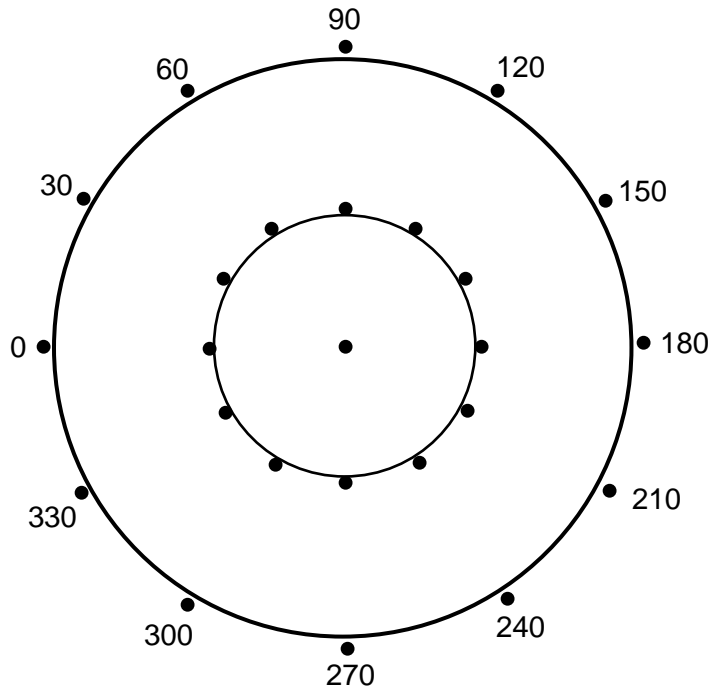Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings



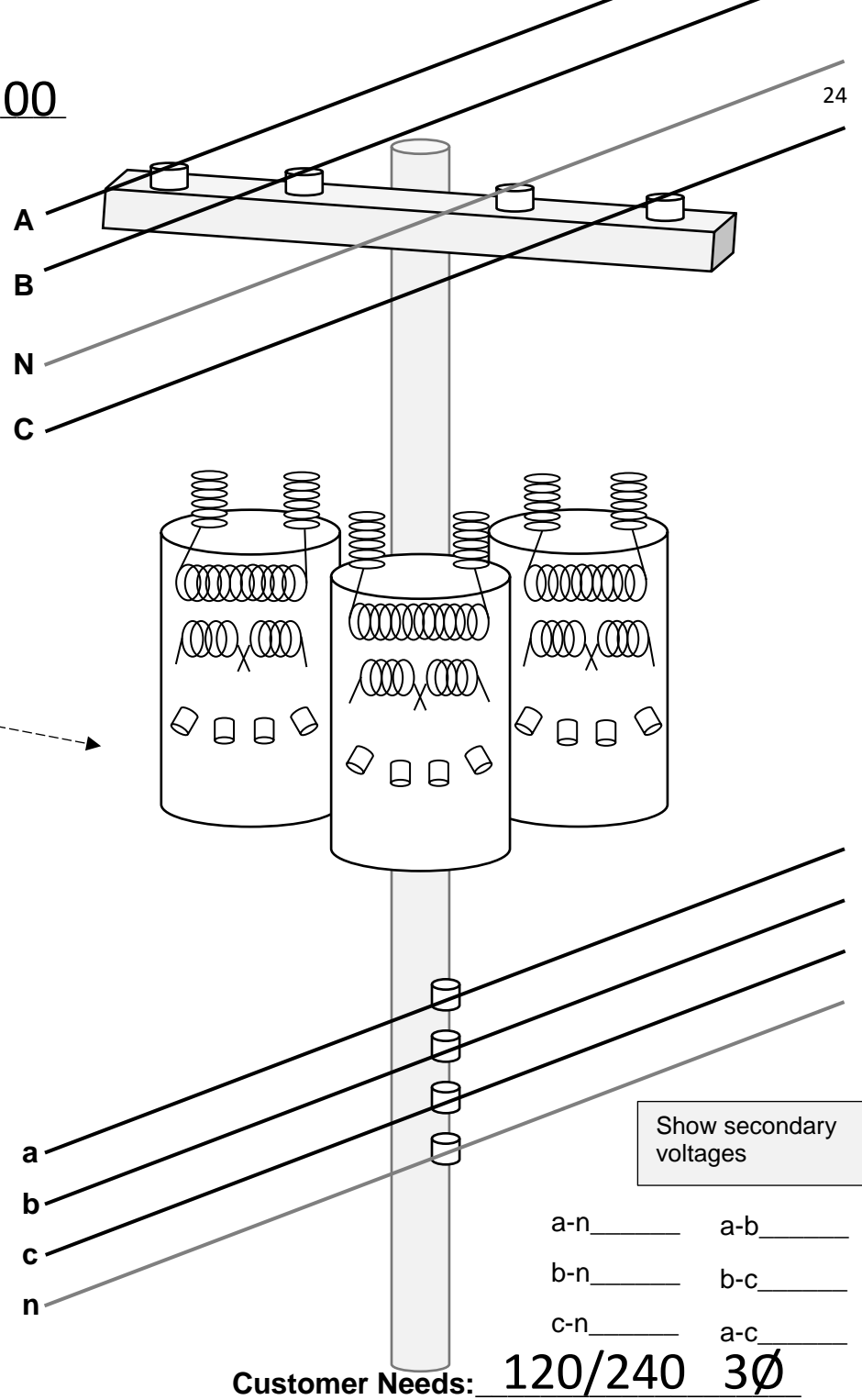Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Show secondary voltages

a-n _____	a-b _____
b-n _____	b-c _____
c-n _____	a-c _____

Customer Needs: 120/240 3Ø

Circuit Voltage: 4160

Connect the Transformer Using the Following Information:

Transformer 1

HV - 2,400 / 4,160v **KVA** - 25 KVA
LV - 277v **POL** -

Transformer 2


HV - 2,400 / 4,160v **KVA** - 25 KVA
LV - 277v **POL** -

Transformer 3


HV - 2,400 / 4,160v **KVA** - 25 KVA
LV - 277v **POL** -

Using industry standards fill in the correct polarity

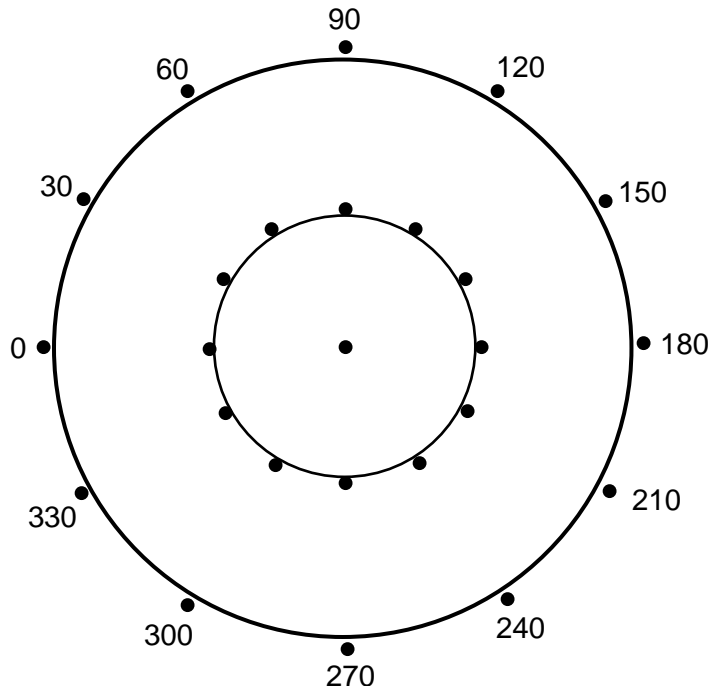Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings



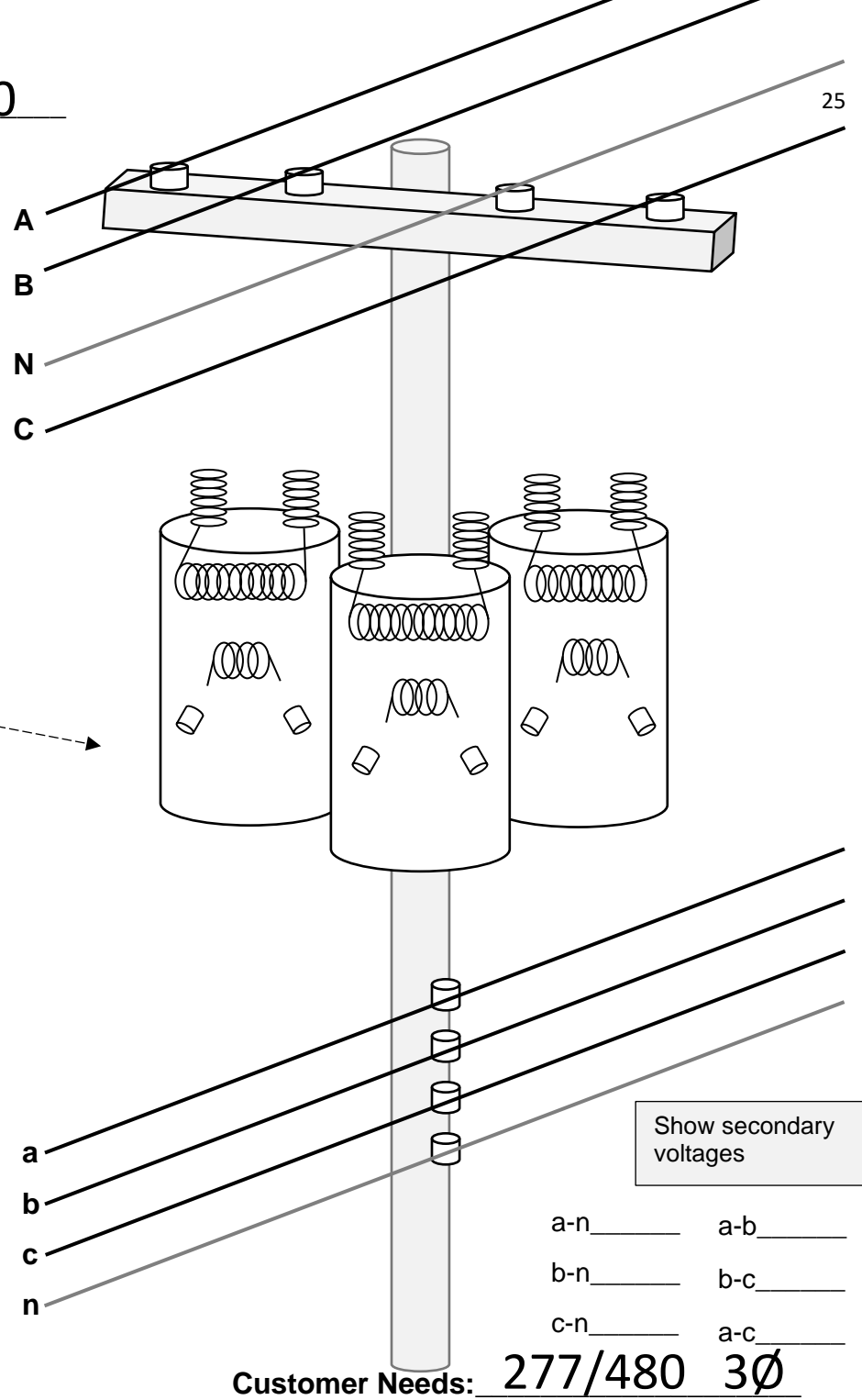Use Outer Circle for Primary Vector - Label A, B, & C
Use Inner Circle for Secondary Vector - Label a, b, & c



Show secondary voltages

a-n _____ a-b _____
b-n _____ b-c _____
c-n _____ a-c _____

Customer Needs: 277/480 3Ø

Circuit Voltage: 34,500

Connect the Transformer Using the Following Information:

Transformer 1

HV – 34,500v KVA - 125 KVA
 LV – 240 / 480v POL -

Transformer 2


HV – 34,500v KVA - 125 KVA
 LV – 240 / 480v POL -

Transformer 3


HV – 34,500v KVA - 125 KVA
 LV – 240 / 480v POL -

Using industry standards fill in the correct polarity

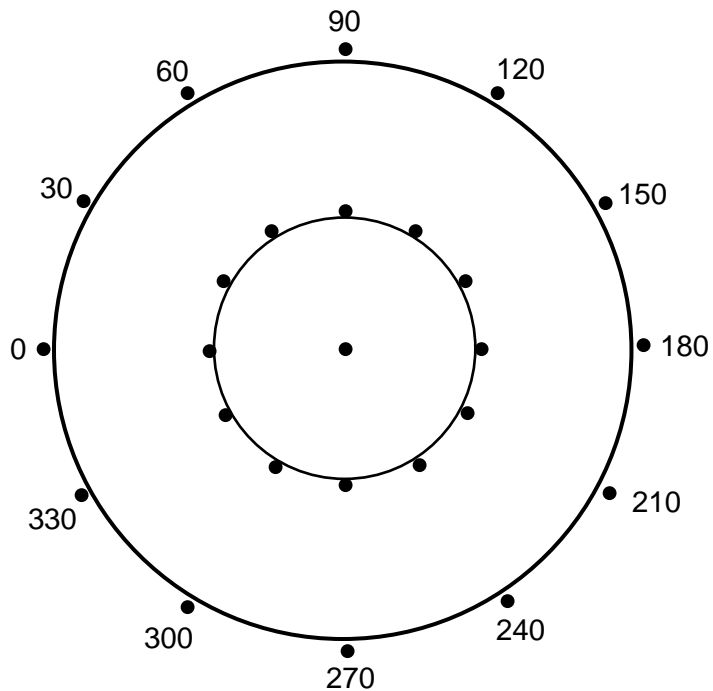Connect the secondary coil leads to the secondary bushings. Label all the "x" bushings



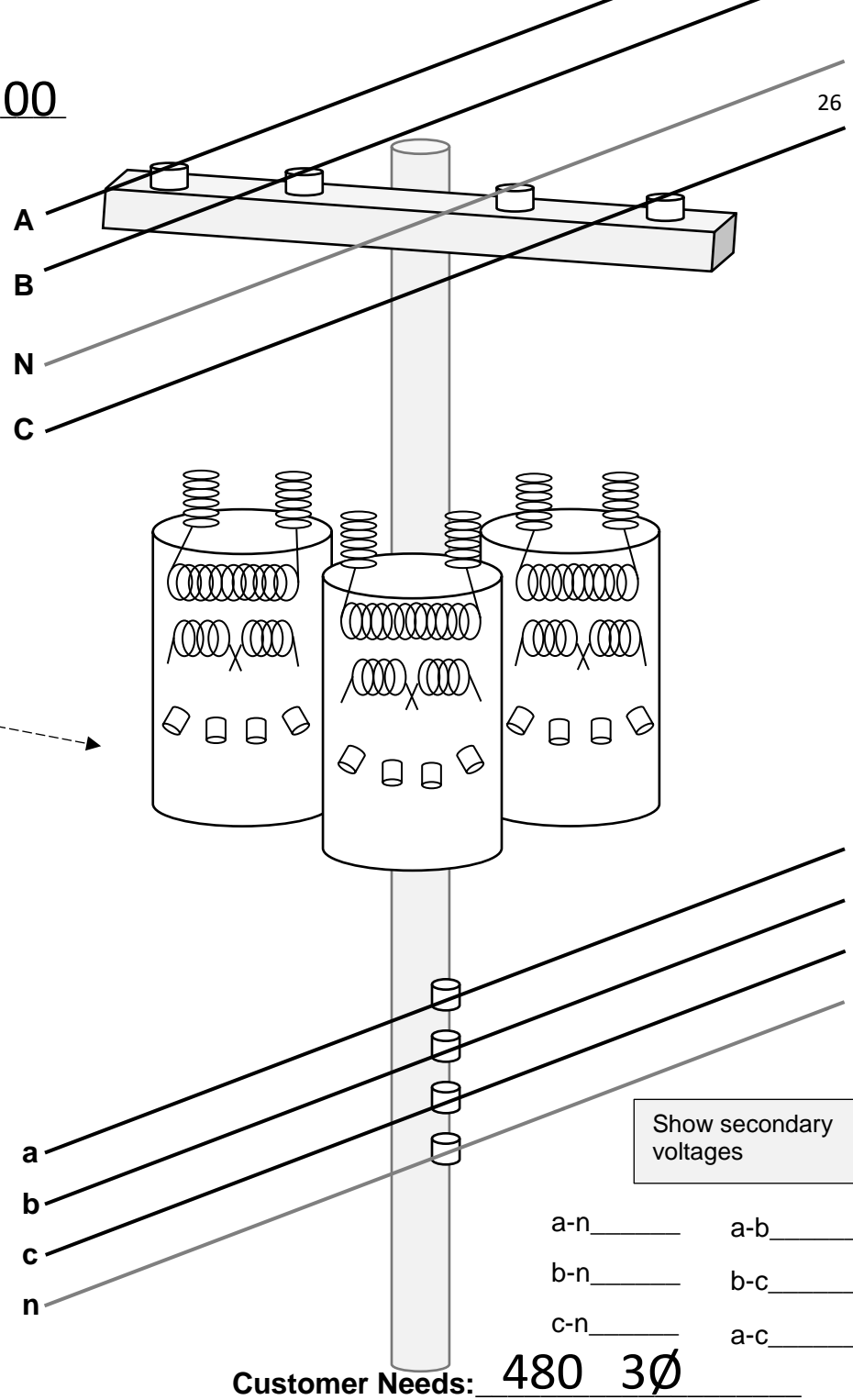Use Outer Circle for Primary Vector - Label A, B, & C
 Use Inner Circle for Secondary Vector - Label a, b, & c



Show secondary voltages

a-n _____ a-b _____
 b-n _____ b-c _____
 c-n _____ a-c _____

Customer Needs: 480 3Ø